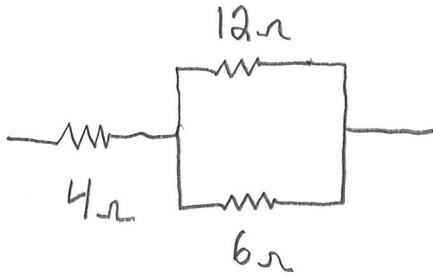


Physics 11 Resistors Practice #2

Name: _____


1. Calculate the equivalent resistance of the circuits drawn below.

a)




$R_{TOTAL} =$ _____

b)

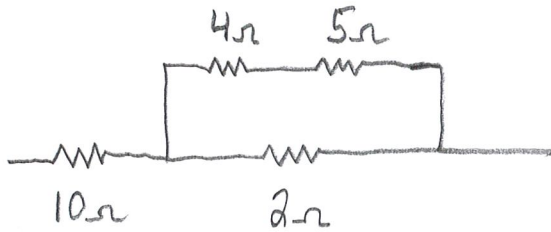


$R_{TOTAL} =$ _____


c)

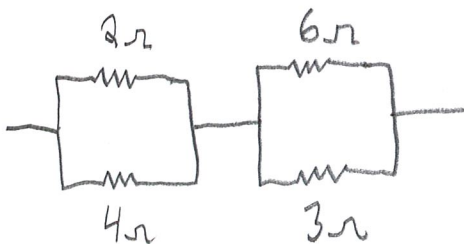


$R_{TOTAL} =$ _____

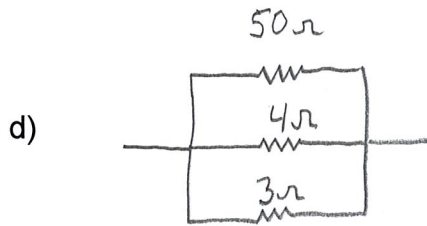

$R_{TOTAL} = \underline{\hspace{2cm}}$

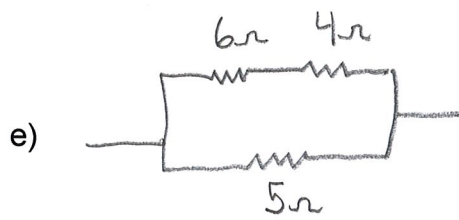

$R_{TOTAL} = \underline{\hspace{2cm}}$

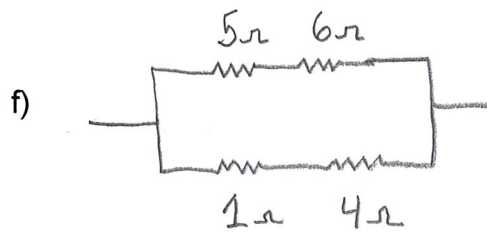

$R_{TOTAL} = \underline{\hspace{2cm}}$