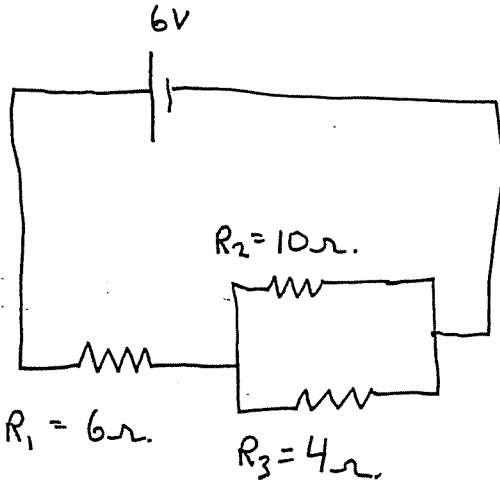


**Physics 12 Chapter 18/19 Circuit Analysis Worksheet #2**

Name: \_\_\_\_\_

1. Find the required missing values. Show your working in clearly defined (boxed) steps.



$$I_1 = \underline{\hspace{2cm}} \quad V_1 = \underline{\hspace{2cm}}$$

$$I_2 = \underline{\hspace{2cm}} \quad V_2 = \underline{\hspace{2cm}}$$

$$I_3 = \underline{\hspace{2cm}} \quad V_3 = \underline{\hspace{2cm}}$$

⑥  $I_2 = \frac{V}{R} = \frac{1.935}{10} = 0.1935 \text{ A}$

⑦  $I_{IN} = I_{OUT}$   
 $0.6774 = I_2 + I_3$   
 $I_3 = 0.4839 \text{ A}$

①  $R_{TOT} = 6 + 2.857 = 8.857$


②  $I_{TOT} = I_1 = \frac{V}{R} = \frac{6}{8.857} = 0.6774 \text{ A}$

③  $V_1 = I_1 R_1 = (0.6774)(6) = 4.064 \text{ A}$

④  $V_{GAIN} = V_{LOSS}$  (for any loop)  
 $6 \text{ V} = V_1 + V_2 \quad V_2 = 1.935 \text{ V}$

⑤  $V_2 = V_3 \quad V_3 = 1.935 \text{ V}$

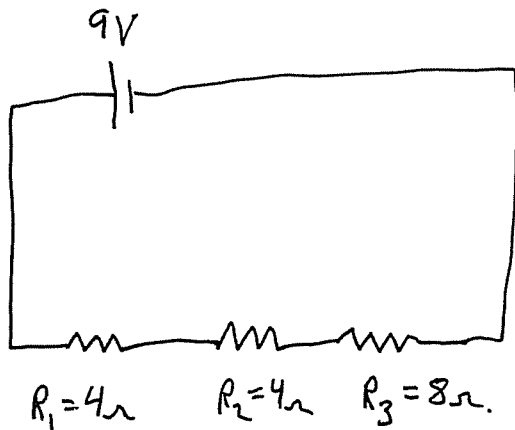2. Find the required missing values. Show your working in clearly defined (boxed) steps.



$$I_1 = \underline{\hspace{2cm}}$$

$$V_1 = \underline{\hspace{2cm}}$$

$$V_3 = \underline{\hspace{2cm}}$$


①  $R_{TOT} = 16 \Omega$

②  $I_{TOT} = I_1 = I_2 = I_3$   
 $= \frac{V}{R} = \frac{9 \text{ V}}{16} = 0.5625 \text{ A}$

③  $V_1 = I R_1 = 2.25 \text{ V}$

$V_3 = I R_3 = 4.5 \text{ V}$

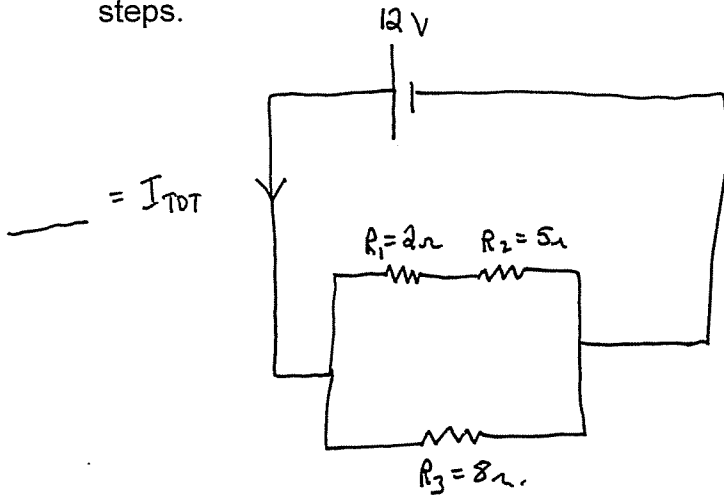3. Find the required missing values. Show your working in clearly defined (boxed) steps.



$$V_1 = \underline{\hspace{2cm}} \quad I_1 = \underline{\hspace{2cm}}$$

$$V_2 = \underline{\hspace{2cm}} \quad I_2 = \underline{\hspace{2cm}}$$

$$V_3 = \underline{\hspace{2cm}} \quad I_3 = \underline{\hspace{2cm}}$$

$$\textcircled{1} R_{TOT} = 3.733\Omega$$

$$\textcircled{2} I_{TOT} = \frac{V}{R} = \frac{12}{3.73} = 3.217 \text{ A}$$

$$\textcircled{3} V_{HIGH} = V_{LOW} \quad \textcircled{4} I_3 = \frac{V_3}{R_3} = \frac{12}{8} = 1.5 \text{ A}$$

$$\textcircled{5} I_{IN} = I_{OUT}$$


$$I_{TOT} = I_1 + I_3 \quad I_1 = 1.717 \text{ A}$$

$$\textcircled{6} V_1 = I_1 R_1 = 3.434 \text{ V}$$

$$V_2 = I_1 R_2 = 8.585$$

$$I_1 = I_2$$

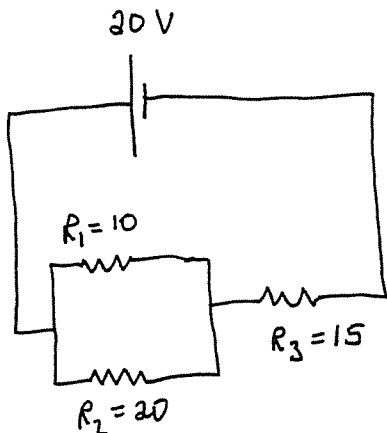4. Find the required missing values. Show your working in clearly defined (boxed) steps.



$$V_1 = \underline{\hspace{2cm}} \quad I_1 = \underline{\hspace{2cm}}$$

$$V_2 = \underline{\hspace{2cm}} \quad I_2 = \underline{\hspace{2cm}}$$

$$V_3 = \underline{\hspace{2cm}} \quad I_3 = \underline{\hspace{2cm}}$$

$$\textcircled{1} R_{TOT} = 21.667\Omega$$

$$\textcircled{2} I_{TOT} = \frac{V}{R} = \frac{20}{21.667} = 0.9231 \text{ A}$$

$$\textcircled{3} V_3 = I R_3 = 13.846 \text{ V}$$

$$\textcircled{4} V_{HIGH} = V_{LOW}$$

$$20 \text{ V} = V_3 + V_1$$

$$V_1 = 6.154 \text{ V} = V_2$$

$$\textcircled{5} I_1 = \frac{V_1}{R_1} = \frac{6.154}{10} = 0.6154$$

$$\textcircled{6} I_2 = \frac{V_2}{R_2} = \frac{6.154}{20} = 0.3077$$

$$\boxed{V_1 = V_2}$$